 


Příklady popisu obvodů ve VHDL

Zdeněk Vašíček, Vojtěch Mrázek, 2021



Úplná sčítačka (dataflow popis)



```
entity FullAdder is  
  port(X, Y, Cin: in bit;    --Inputs  
        Cout, Sum: out bit);  --Outputs  
end FullAdder;
```


```
architecture dataflow of FullAdder is  
begin
```

```
  Sum  <= X xor Y xor Cin after 1 ns;  
  Cout <= '1' when (X and Y) or (X and Cin) or (Y and Cin) else  
          '0' after 1 ns;
```

```
end architecture;
```

- využíváme pouze konstrukce přiřazení signálů
- lze uvést podmínku (when) – vhodné pro popis multiplexoru, dekodéru, ...
případně přiřadit zpoždění (after) – pro potřeby simulace

4-bitová sčítačka (strukturní popis)

 

```
entity Adder4 is
  port(
    A, B: in std_logic_vector(3 downto 0);
    Ci: in std_logic;
    S: out std_logic_vector(3 downto 0);
    Co: out std_logic);
end Adder4;
```


```
architecture structure of Adder4 is
  component FullAdder
    port(X, Y, Cin: in std_logic; Cout, Sum: out std_logic);
  end component;
  signal C: std_logic_vector(3 downto 1);
begin

  FA0: FullAdder port map(A(0), B(0), Ci, C(1), S(0));
  FA1: FullAdder port map(A(1), B(1), C(1), C(2), S(1));
  FA2: FullAdder port map(A(2), B(2), C(2), C(3), S(2));
  FA3: FullAdder port map(X <= A(3), Y <= B(3),
    Cin <= C(3),
    Sum <= S(3), Cout <= Co);

end structure;
```

využití konstrukce
component a **port map**
(poziční ne/závislost)
analogie konstrukce
číslicových systémů ze
součástek – propojování
komponent (součástek)
signály (dráty)
komponenta jako blackbox
– pracovat může více
vývojářů současně

4-bitová sčítačka (behaviorální popis)

 

```
entity Adder4 is
  port(
    A, B: in std_logic_vector(3 downto 0);
    Ci: in std_logic;
    S: out std_logic_vector(3 downto 0);
    Co: out std_logic);
end Adder4;
```

```
architecture behavioral of Adder4 is
  Begin
```



```
    process (A,B,Ci)
      variable t: std_logic_vector(4 downto 0);
    begin
      t := ('0'&A) + ('0'&B) + Ci;
      S <= t(3 downto 0);
      Co <= t(4);
    end process;
  end behavioral;
```

```
use IEEE.std_logic_unsigned.all;
```

- využití procesů
- pozor na sensitivity list
(v případě kombinační funkce musí být uveden seznam všech signálů ze kterých je odvozen výsledek)



Koncept zpoždění
  
```
process (CLK) is
begin
  if rising_edge(CLK) then
    Q <= Q + 1;
  end if;
end process;
```



Koncept zpoždění
  
```
process (CLK) is
begin
  if rising_edge(CLK) then
    Q <= Q + 1;
  end if;
end process;
```



Co by se stalo, když by sčítání trvalo delší dobu?


Co dělat, když se nejdelší cesta je delší než perioda T?

Návrh obvodu realizujícího iterační součet posloupnosti

- Cílem je navrhnout primitivní obvod, který je schopen vypočítat součet hodnot N (např. 8) prvků umístěných v paměti.
- Praktické použití (po rozšíření): kontrola a generování CRC součtu

```
const N = 8
char mem[N] = {1,...};
char i
char sum;

 sum = 0
for (i=0;i<N;i++)
    sum += mem[i]
```



- Jak převedeme pseudo kód na HW implementaci?
Stačí umět převést sekvenci, selekci, iteraci.


Implementace základních konstrukcí v SW a HW

sekvence (posloupnost operací)

Sekvence příkazů

```
A = B + C  
D = sin(A)  
Y = F(D)
```

(3 kroky)

 

Implementace základních konstrukcí v SW a HW

selekce (větvení výpočtu)

Podmíněné vykonávání


```
If (S == 0):  
    Y = F(X)  
else:  
    Y = G(X)
```

(3/4 instrukce CPU)

VS.

```
Y = G(X)  
If (S == 0):  
    Y = F(X)
```

(3/5 instrukce CPU)

 


Implementace základních konstrukcí v SW a HW

iterace (opakování výpočtu)

Iterativní zpracování (smyčky)


```
sum = 0  
i = 0  
while (i < 8):  
    sum = sum + mem[i]  
    i += 1
```

(cca 40 instrukcí CPU)

 

Obvod realizující iterační součet posloupnosti

- Čítač (Cnt) generuje adresy celého rozsahu paměti (Mem), zastaví se u adresy 7
- Hodnoty (val) z paměti jsou sčítány sčítačkou (Add) a mezivýsledek uchován v registru (Reg)
- Signál EN, zabraňující přepsání finálního výsledku v Reg, je deaktivován po vygenerování nejvyšší adresy paměti
- Signál RST v log. 1 způsobí nulování registru a čítače
- CLK synchronizuje činnost sekvenčních obvodů – čítače a registru
- Po kompletním průchodu pamětí obsahuje Reg (a jeho výstup – signál SUM) součet všech jejích hodnot a signál DONE je aktivní (v log. 0)

 

Založení projektu ISE

Základní práce s nástroji Xilinx

Instalace, spuštění, založení projektu, spuštění testu

Vojtěch Mrázek
mrazek@fit.vutbr.cz



<https://www.youtube.com/watch?v=7YMqNoJDi3M>

Sekvenční sčítačka s využitím komponent

(strukturní popis)

```
entity Acc is
  port (
    CLK: in std_logic;
    RST: in std_logic;
    SUM: out std_logic_vector(7 downto 0);
    DONE: out std_logic
  );
end Acc;

architecture struct of Acc is
  component Add is
    port (
      A: in std_logic_vector(7 downto 0);
      B: in std_logic_vector(7 downto 0);
      RES: out std_logic_vector(7 downto 0)
    );
  end component;

  component Cnt is
    port (
      CLK: in std_logic;
      RST: in std_logic;
      ADDR: out std_logic_vector(2 downto 0);
      STOP: out std_logic
    );
  end component;

  component Mem is
    port (
      ADDR: in std_logic_vector(2 downto 0);
      VAL: out std_logic_vector(7 downto 0)
    );
  end component;
```


```
  component Reg is
    port (
      CLK: in std_logic;
      RST: in std_logic;
      EN: in std_logic;
      DIN: in std_logic_vector(7 downto 0);
      DOUT: out std_logic_vector(7 downto 0)
    );
  end component;

  signal addr: std_logic_vector(2 downto 0);
  signal val: std_logic_vector(7 downto 0);
  signal add_out: std_logic_vector(7 downto 0);
  signal reg_out: std_logic_vector(7 downto 0);
  signal en: std_logic;

begin

  add_inst: Add port map(A => val, B => reg_out, RES => add_out);
  mem_inst: Mem port map(ADDR => addr, VAL => val);
  cnt_inst: Cnt port map(CLK, RST, addr, en);
  reg_inst: Reg port map(CLK, RST, en, add_out, reg_out);

   SUM <= reg_out;
  DONE <= en;
end struct;
```




Model sčítačky (komponenta Add)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;

entity Add is
port (
  A: in std_logic_vector(7 downto 0);
  B: in std_logic_vector(7 downto 0);
  RES: out std_logic_vector(7 downto 0)
);
end Add;

 
architecture behav_add of Add is
begin
  RES <= A + B;
end behav_add;
```



Model čítače (komponenta Cnt)

```
entity Cnt is  
port (  
    CLK: in std_logic;  
    RST: in std_logic;  
    ADDR: out std_logic_vector(2 downto 0);  
    EN: out std_logic  
);  
end Cnt;
```

```
architecture behav of Cnt is  
signal cnt: std_logic_vector(2 downto 0);  
begin  
    cnt_proc: process (CLK, RST)  
    begin  
        if RST = '1' then  
            cnt <= "000";  
            EN <= '1';  
        elsif CLK'event and CLK = '1' then  
            EN <= '1';  
            if cnt = "111" then  
                EN <= '0';  
            else  
                cnt <= cnt + 1;  
            end if;  
        end if;  
    end process;  
  
    ADDR <= cnt;  
end behav;
```

 


Model ROM paměti (komponenta Mem)

```
entity Mem is
port (
  ADDR: in std_logic_vector(2 downto 0);
  VAL: out std_logic_vector(7 downto 0)
);
end Mem;

architecture behav_mem of Mem is


begin
  mem: process (ADDR)
  begin
    case ADDR is
      when "000" => VAL <= "00000001";
      when "001" => VAL <= "00000010";
      when "010" => VAL <= "00000011";
      when "011" => VAL <= "00000111";
      when "100" => VAL <= "00001111";
      when "101" => VAL <= "00011111";
      when "110" => VAL <= "00111111";
      when "111" => VAL <= "01111111";
      when others => VAL <= "00000000";
    end case;
  end process;
end behav_mem;
```

 

Model registru (komponenta Reg)

```
entity Reg is
port (
  CLK: in std_logic;
  RST: in std_logic;
  EN: in std_logic;
  DIN: in std_logic_vector(7 downto 0);
  DOUT: out std_logic_vector(7 downto 0)
);
end Reg;

 architecture behav of Reg is
begin
  reg: process (CLK, RST)
  begin
    if RST = '1' then
      DOUT <= "00000000";
    elsif CLK'event and CLK = '1' then
      if EN='1' then
        DOUT <= DIN;
      end if;
    end if;
  end process;
end behav;
```




Model registru (komponenta Reg)

 Příklad využití generických proměnných

```
entity Reg is
generic (
    DATA_WIDTH : integer := 8
)
port (
    CLK: in std_logic;
    RST: in std_logic;
    EN: in std_logic;
    DIN: in std_logic_vector(DATA_WIDTH-1 downto 0);
    DOUT: out std_logic_vector(DATA_WIDTH-1 downto 0)
);
end Reg;

architecture behav of Reg is
begin
    reg: process (CLK, RST)
    begin
        if RST = '1' then
            DOUT <= (others => '0');
        elsif CLK'event and CLK = '1' then
            if EN='1' then
                DOUT <= DIN;
            end if;
        end if;
    end process;
end behav;
```



Sekvenční sčítačka popsaná behaviorálně

```
entity Acc is
port (
  CLK: in std_logic;
  RST: in std_logic;
  SUM: out std_logic_vector(7 downto 0);
  DONE: out std_logic
);
end Acc;

architecture behav of Acc is

  signal addr: std_logic_vector(2 downto 0);
  signal val: std_logic_vector(7 downto 0);
  signal add_out: std_logic_vector(7 downto 0);
  signal reg_out: std_logic_vector(7 downto 0);
  signal stop: std_logic;

begin
  cnt: process(CLK, RST)
  begin
    if RST = '1' then
      addr <= "000";
      stop <= '0';
    elsif clk'event and clk = '1' then
      if addr = "111" then
        stop <= '1';
      else
        addr <= addr + 1;
        stop <= '0';
      end if;
    end if;
  end if;
end process;

  with addr select
    val <= "00000001" when "000",
           "00000010" when "001",
           "00000011" when "010",
           "00000111" when "011",
           "00001111" when "100",
           "00011111" when "101",
           "00111111" when "110",
           "01111111" when "111",
           "00000000" when others;
```

```
reg: process(CLK, RST)
begin
  if RST = '1' then
    reg_out <= X"00";
  elsif clk'event and clk = '1'
  then
    if stop = '0' then
      reg_out <= add_out;
    end if;
  end if;
end process;

  add_out <= reg_out + val;


  SUM <= reg_out;
  DONE <= not stop;
end behav;
```

```
graph TD
    RST --> Cnt
    RST --> Reg
    CLK --> Cnt
    CLK --> Reg
    Cnt -- addr --> Mem
    Mem -- val --> Add
    Reg -- reg_out --> Add
    Add -- add_out --> Reg
    Reg -- SUM --> SUM
    Reg -- DONE --> DONE
    Reg -- reg_out --> reg_out
```

Připomenutí principů modelování konečných automatů ve VHDL


Typy konečných automatů

 - Obvod mající paměť lze chápat jako konečný stavový automat (FSM)
- Návrh automatu vyžaduje
 - definovat stavy automatu, přechody mezi stavy a výstupní funkci
- Podle způsobu realizace výstupu rozlišujeme dva základní FSM
 - Moore (výstup je pouze funkcí stavu),
 - Mealy (výstup je funkcí stavu a vstupů)



Typy konečných automatů

 
- Obvod mající paměť lze chápat jako konečný stavový automat (FSM)
- Návrh automatu vyžaduje
 - definovat stavy automatu, přechody mezi stavy a výstupní funkci
- Podle způsobu realizace výstupu rozlišujeme dva základní FSM
 - Moore (výstup je pouze funkcí stavu),
 - **Mealy** (výstup je funkcí stavu a vstupů)




Implementace konečných automatů ve VHDL

 Příklad: detektor posloupnosti 10

- VHDL implementace konečných automatů
 - FSM lze ve VHDL popsat pomocí dvou nebo tří procesů
- Příklad FSM: detektor posloupnosti 10 v řetězci
 - výstupem je 1 pokud byla detekována posloupnost 10



Detektor – Moore FSM – 2 procesy

 

Deklarace signálů

```
type FSMstate is (SXX, SX1, S10);
signal pstate : FSMstate;
signal nstate : FSMstate;
```

```
--Present State register
pstatereg: process(RST, CLK)
begin
    if (RST='1') then
        pstate <= SXX;
    elsif (CLK'event) and (CLK='1') then
        pstate <= nstate;
    end if;
end process;
```

```
--Next State logic + output logic
nstate_logic: process(pstate, A)
begin
    nstate <= SXX;
    Y <= '0';
    case pstate is
        when SXX =>
            if (A = '1') then
                nstate <= SX1;
            end if;
        when SX1 =>
            nstate <= SX1;
            if (A = '0') then
                nstate <= S10;
            end if;
        when S10 =>
            nstate <= SX1;
            Y <= '1';
            if (A = '0') then
                nstate <= SXX;
            end if;
        when others => null;
    end case;
end process;
```


Detektor – Moore FSM – 3 procesy

```
--Present State register
pstatereg: process(RST, CLK)
begin
    if (RST='1') then
        pstate <= SXX;
    elsif (CLK'event) and (CLK='1') then
        pstate <= nstate;
    end if;
end process;
```

```
--Output logic
output_logic: process(pstate)
begin
    Y <= '0';
    case pstate is
        when S10 =>
            Y <= '1';
        when others => null;
    end case;
end process;
```

```
--Next State logic
nstate_logic: process(pstate, A)
begin
    nstate <= SXX;
    case pstate is
        when SXX =>
            if (A = '1') then
                nstate <= SX1;
            end if;
        when SX1 =>
            nstate <= SX1;
            if (A = '0') then
                nstate <= S10;
            end if;
        when S10 =>
            nstate <= SX1;
            if (A = '0') then
                nstate <= SXX;
            end if;
        when others => null;
    end case;
end process;
```

Detektor – Mealy FSM – 2 procesy

 

Deklarace signálů

```
type FSMstate is (S0, S1);  
signal pstate : FSMstate;  
signal nstate : FSMstate;
```

```
--Present State register  
pstatereg: process(RST, CLK)  
begin  
    if (RST='1') then  
        pstate <= S0;  
    elsif (CLK'event) and (CLK='1') then  
        pstate <= nstate;  
    end if;  
end process;
```

```
--Next State logic + output logic  
nstate_logic: process(pstate, A)  
begin  
    nstate <= S0;  
    Y <= '0';  
    case pstate is  
        when S0 =>  
            if (A = '1') then  
                nstate <= S1;  
            end if;  
        when S1 =>  
            nstate <= S1;  
            if (A = '0') then  
                Y <= '1';  
                nstate <= S0;  
            end if;  
        when others => null;  
    end case;  
end process;
```

Detektor – Mealy FSM – 3 procesy

```
--Present State register
pstatereg: process(RST, CLK)
begin
    if (RST='1') then
        pstate <= S0;
    elsif (CLK'event) and (CLK='1') then
        pstate <= nstate;
    end if;
end process;
```

```
--Output logic
output_logic: process(pstate, A)
begin
    Y <= '0';
    if (pstate = S1) and (A = 0) then
        Y <= '1';
    end if;
end process;
```

```
--Next State logic + output logic

nstate_logic: process(pstate, A)
begin
    nstate <= S0;
    case pstate is
        when S0 =>
            if (A = '1') then
                nstate <= S1;
            end if;
        when S1 =>
            nstate <= S1;
            if (A = '0') then
                nstate <= S0;
            end if;
        when others => null;
    end case;
end process;
```

Pozor na sensitivity list u výstupní logiky

Detektor – Mealy FSM – 3 procesy

```
--Present State register
pstatereg: process (RST, CLK)
begin
    if (RST='1') then
        pstate <= S0;
    elsif (CLK'event) and (CLK='1') then
        pstate <= nstate;
    end if;
end process;
```

Výstupní logika nemusí být nutně popsána pomocí procesu

```
--Output logic
Y <= '1' when (pstate = S1) and (A = 0) else
    '0';
```

```
--Next State logic + output logic

nstate_logic: process (pstate, A)
begin
    nstate <= S0;
    case pstate is
        when S0 =>
            if (A = '1') then
                nstate <= S1;
            end if;
        when S1 =>
            nstate <= S1;
            if (A = '0') then
                nstate <= S0;
            end if;
        when others => null;
    end case;
end process;
```